

Digital Logic Circuits  
'Performance Analysis'  
ELEC2200  
Summer 2009

David J. Broderick  
[brodedj@auburn.edu](mailto:brodedj@auburn.edu)  
<http://www.auburn.edu/~brodedj>  
Office: Broun 360



# You Are Here

- We can:
  - Represent real values with binary numbers
  - Use Boolean algebra to manipulate binary expressions (minimize)
  - Use K-maps to find minimal SOP/POS expression
  - Once you have an expression, draw the circuit
  - Reconstruct the truth table and expression given a circuit
- We're left with what's the difference between a good circuit and a great circuit?




# Area Analysis

- How small will the circuit be?
  - # of gates
    - More gates, bigger circuit
  - # of inputs and outputs to all gates
    - Adding inputs make a gate bigger
    - More inputs/outputs, bigger circuit

- $Z=(A+B')C+A'BC'$


- $G=7$

- $G_{IO}=19$

 
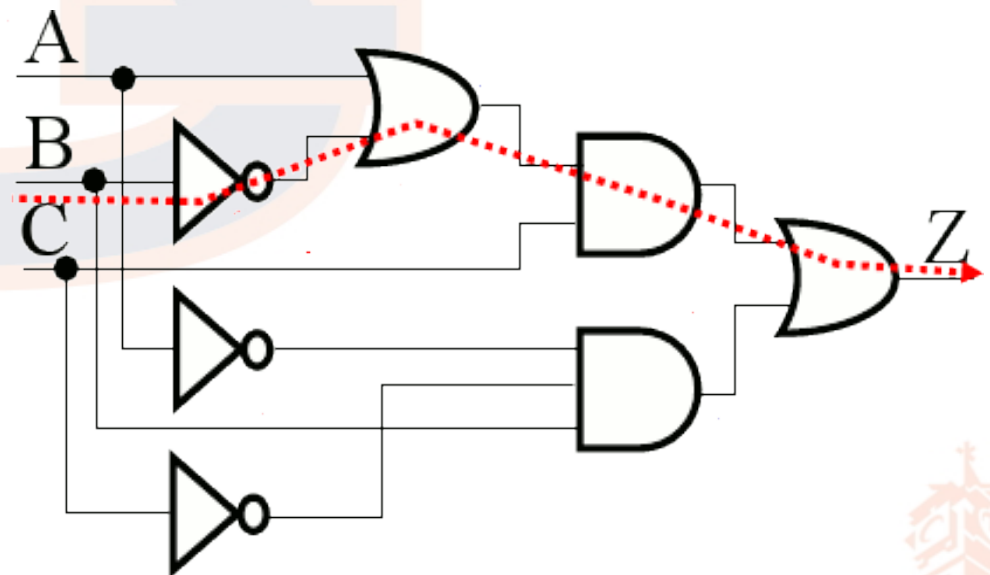
# Performance Analysis

- How fast will the circuit switch states?
- In the worst case, how long does it take for a change in the inputs to cause a change in the output?
- Gate Delay
  - # of gates between input and output in the worst case path
- $Z = (A + B')C + A'BC'$
- $G_{del} = 4$
- Worst case path =  $B \rightarrow Z$




# Performance Analysis

- Propagation Delay, a more accurate measure
- Propagation Delay = intrinsic delay + extrinsic delay
- Relative Propagation Delay = # of inputs to gate (intrinsic) + # of loads on gate (extrinsic)
- Assume all gates fabricated with similar design


 
# Performance Analysis

- Still dealing with worst case path, though it may be different
- Add the number of inputs + number of outputs to a gate
- Add these values through the worst case path
- $Z = (A + B')C + A'BC'$
- $P_{del} = 12$
- Worst case path =  $B \rightarrow Z$



# Performance Metrics

- Area Analysis
  - # of gates ( $G$ ): Most common
  - # of gate input/outputs ( $G_{io}$ ): More accurate
- Performance Analysis (worst case path)
  - How quickly does change in inputs propagate to change in output?
  - # of gates in worst case path ( $G_{del}$ )
  - Propagation Delay: More accurate measure of delay



# Performance Metrics

- A look a XOR circuits

- MSOP Form

- $G=5$


- $G_{IO}=13$

- Worst case:

- Either path

- $G_{del}=3$

- $P_{del}=9$

 



# Performance Metrics

- A look a XOR circuits

- NAND-NAND

- $G=4$


- $G_{IO}=12$

- Worst case:

- Either path

- $G_{del}=3$

- $P_{del}=11$

 

# Performance Metrics

- A look a XOR circuits

- $G=3$


- $G_{IO}=9$

- Worst case:

- Either path

- $G_{del}=2$

- $P_{del}=7$

 

# XOR Performance

- MSOP is a good start
- NAND-NAND makes circuit smaller at cost of performance
- 3<sup>rd</sup> circuit minimizes both area and performance
- **Don't assume the MSOP is an optimized circuit!**



# Circuit Optimization

- We want smallest, fastest circuit
- Basic Goals
  - Minimize the # of product terms
  - Minimize the # of literals
- K-maps a very effective tool
- Further optimization possible with Boolean algebra

